

Lab 2

Question 1

Behavioral Modelling Code

```
// Q1_bcd_9scomp.v
module Q1_bcd_9scomp(
    input  [3:0] bcd_in,
    output reg [3:0] comp
);

always @(*) begin
    if (bcd_in ≤ 9)
        comp = 9 - bcd_in;
    else
        comp = 4'bxxxx;
end

endmodule
```

Testbench

```
`timescale 1ns/1ps

module Q1_bcd_9scomp_tb;

reg [3:0] bcd_in;
wire [3:0] comp;

Q1_bcd_9scomp uut (
    .bcd_in(bcd_in),
    .comp(comp)
);

initial begin
    $display("Time | BCD Input | 9's Complement");
    $monitor("%4t |      %d      |          %d", $time, bcd_in, comp);


    // Test all valid BCD digits (0-9)
    bcd_in = 0; #10;
    bcd_in = 1; #10;
    bcd_in = 2; #10;
    bcd_in = 3; #10;
    bcd_in = 4; #10;
    bcd_in = 5; #10;
    bcd_in = 6; #10;
    bcd_in = 7; #10;
    bcd_in = 8; #10;
    bcd_in = 9; #10;

    // Test invalid input
    bcd_in = 10; #10;
    bcd_in = 15; #10;

    $finish;
end

endmodule
```

Output

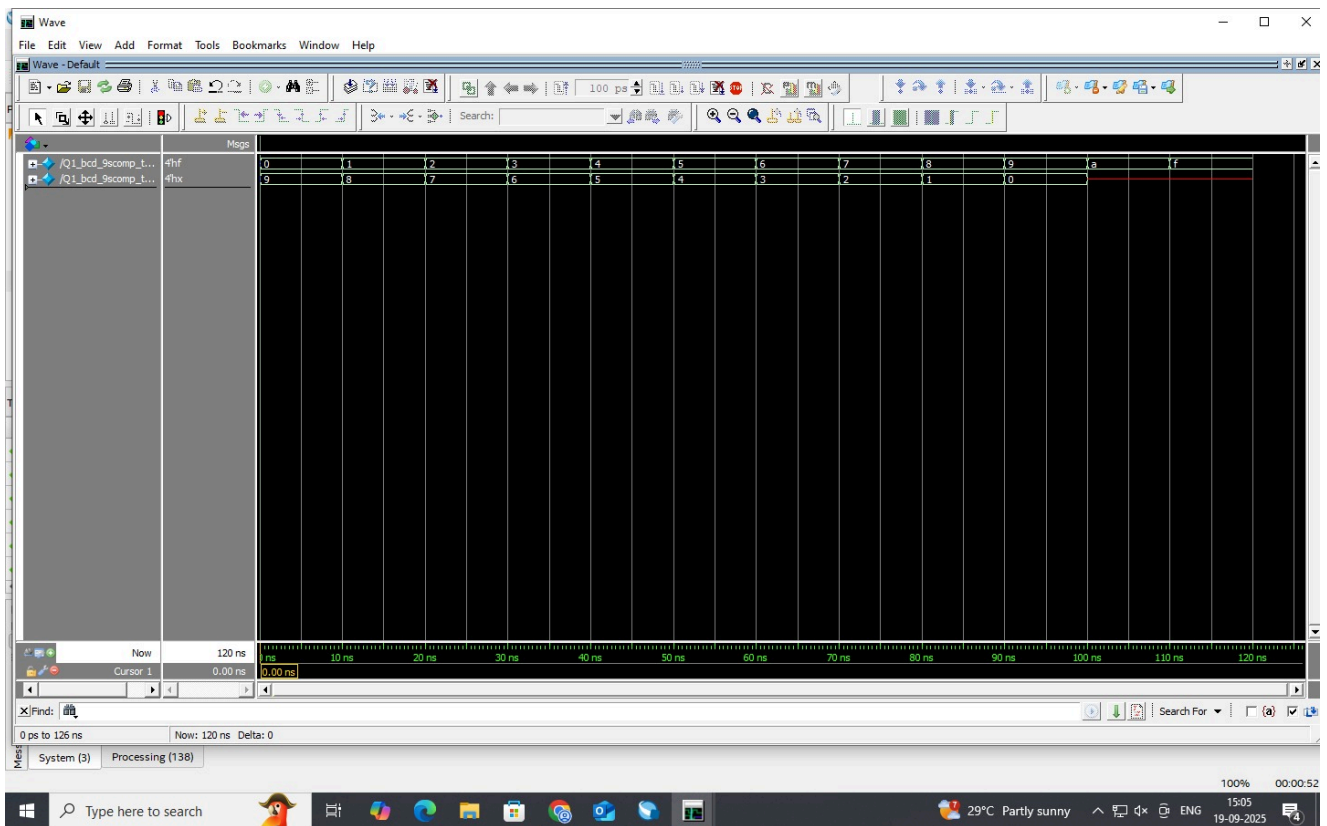

Question 2

Gate Modelling Code

```
module Q2_priority_encoder_gate(D, x, y, v);
    input  [3:0] D;    // D[3] highest priority
    output x, y, v;

    wire notD2, and1;

    not (notD2, D[2]);
    and (and1, D[1], notD2);
    or  (y, D[3], and1);

    or  (x, D[3], D[2]);
    or  (v, D[3], D[2], D[1], D[0]);
endmodule
```

Behavioral Modelling Code

```
// Q2_priority_encoder_behavioral.v
module Q2_priority_encoder_behavioral(D, x, y, v);
    input  [3:0] D;
    output reg x, y, v;

    always @(*) begin
        v = 1;
        if (D[3]) begin
            x = 1; y = 1;    // 11
        end else if (D[2]) begin
            x = 1; y = 0;    // 10
        end else if (D[1]) begin
            x = 0; y = 1;    // 01
        end else if (D[0]) begin
            x = 0; y = 0;    // 00
        end else begin
            v = 0;           // no valid input
            x = 0; y = 0;
        end
    end
end
endmodule
```

Testbench

```
// Q2_priority_encoder_tb.v
`timescale 1ns/1ps

module Q2_priority_encoder_tb;
    reg [3:0] D;
    wire x_gate, y_gate, v_gate;
    wire x_beh, y_beh, v_beh;

    // Gate-level model
    Q2_priority_encoder_gate uut_gate (D, x_gate, y_gate, v_gate);


    // Behavioral model
    Q2_priority_encoder_behavioral uut_beh (D, x_beh, y_beh, v_beh);

    initial begin
        $display(" D3 D2 D1 D0 | Gate(x y v) | Beh(x y v)");
        $monitor(" %b %b %b %b | %b %b %b | %b %b %b",
            D[3], D[2], D[1], D[0],
            x_gate, y_gate, v_gate,
            x_beh, y_beh, v_beh);


        // All combinations
        D=4'b0000; #10;
        D=4'b0001; #10;
        D=4'b0010; #10;
        D=4'b0011; #10;
        D=4'b0100; #10;
        D=4'b0101; #10;
        D=4'b0110; #10;
        D=4'b0111; #10;
        D=4'b1000; #10;
        D=4'b1001; #10;
        D=4'b1010; #10;
        D=4'b1011; #10;
        D=4'b1100; #10;
        D=4'b1101; #10;
        D=4'b1110; #10;
        D=4'b1111; #10;

        $finish;
    end
endmodule
```

Gate Modelling Output

 

Dataflow Modelling Output

 

Question 3

Code

```
module Q3_quadruple_2_1_mux (  
    input [3:0] A,  
    input [3:0] B,  
    input S,  
    input E,  
    output [3:0] Y  
);  
  
    assign Y = E ? (S ? B : A) : 4'b0000;  
  
endmodule
```

Testbench

```
//Q3_quadruple_2_1_mux_tb.v
`timescale 1ns/1ps

module Q3_quadruple_2_1_mux_tb;

    reg [3:0] A_tb, B_tb;
    reg S_tb, E_tb;
    wire [3:0] Y_tb;

    Q3_quadruple_2_1_mux dut (A_tb, B_tb, S_tb, E_tb, Y_tb);

    initial begin
        $display(" Time | A      | B      | S | E | Y_Output");
        $monitor("%4t | %b | %b | %b | %b | %b",
            $time, A_tb, B_tb, S_tb, E_tb, Y_tb);

        A_tb = 4'b1010;
        B_tb = 4'b0101;

        E_tb = 1'b0; S_tb = 1'b0; #10;

        E_tb = 1'b0; S_tb = 1'b1; #10;

        E_tb = 1'b1; S_tb = 1'b0; #10;

        E_tb = 1'b1; S_tb = 1'b1; #10;

        A_tb = 4'b1111;
        B_tb = 4'b0000;

        E_tb = 1'b1; S_tb = 1'b0; #10;

        E_tb = 1'b1; S_tb = 1'b1; #10;

        $finish;
    end
endmodule
```


Output



Question 4

```
// 1-bit full adder

module full_adder(
    input a, b, cin,
    output sum, cout
);
assign sum = a ^ b ^ cin;
assign cout = (a & b) | (b & cin) | (a & cin);
endmodule
```

```
module ripple_adder4(
    input [3:0] a, b,
    input cin,
    output [3:0] sum,
    output cout
);
wire c1, c2, c3;

full_adder fa0(.a(a[0]), .b(b[0]), .cin(cin), .sum(sum[0]), .cout(c1));
full_adder fa1(.a(a[1]), .b(b[1]), .cin(c1), .sum(sum[1]), .cout(c2));
full_adder fa2(.a(a[2]), .b(b[2]), .cin(c2), .sum(sum[2]), .cout(c3));
full_adder fa3(.a(a[3]), .b(b[3]), .cin(c3), .sum(sum[3]), .cout(cout));
endmodule
```

```
module bcd_correction(  
    input [3:0] sum,  
    input cout,  
    output correction  
);  
// use simple numeric comparison for clarity and correctness  
assign correction = cout | (sum > 4'd9);  
endmodule
```

Code

```
module Q4_bcd_adder(
    input [3:0] A, B,
    input Cin,
    output [3:0] SUM,
    output Cout
);
wire [3:0] sum1;
wire carry1, correction;
wire [3:0] add_corr;

// First 4-bit addition
ripple_adder4 adder1(
    .a(A),
    .b(B),
    .cin(Cin),
    .sum(sum1),
    .cout(carry1)
);

// Correction flag
bcd_correction correct(
    .sum(sum1),
    .cout(carry1),
    .correction(correction)
);

// If correction required, add 6 (0110), else add 0
assign add_corr = correction ? 4'b0110 : 4'b0000;

// Final addition (sum + correction)
ripple_adder4 adder2(
    .a(sum1),
    .b(add_corr),
    .cin(1'b0),
    .sum(SUM),
    .cout(Cout)
);
endmodule
```

Testbench

```
`timescale 1ns/1ps
module Q4_bcd_adder_tb;
reg [3:0] A, B;
reg Cin;
wire [3:0] SUM;
wire Cout;

// Instantiate the top module
Q4_bcd_adder uut (
    .A(A),
    .B(B),
    .Cin(Cin),
    .SUM(SUM),
    .Cout(Cout)
);

initial begin
$display("time\tA B Cin | SUM Cout");
$monitor("%0t\t%0d %0d %b | %0d %b", $time, A, B, Cin, SUM, Cout);

A = 4'd0; B = 4'd0; Cin = 0; #10;
A = 4'd5; B = 4'd7; Cin = 0; #10; // expect 12 → SUM=2, Cout=1
A = 4'd3; B = 4'd6; Cin = 1; #10; // 3+6+1=10 → SUM=0, Cout=1
A = 4'd9; B = 4'd9; Cin = 0; #10; // 18 → SUM=8, Cout=1
A = 4'd9; B = 4'd9; Cin = 1; #10; // 19 → SUM=9, Cout=1
A = 4'd2; B = 4'd8; Cin = 1; #10; // 11 → SUM=1, Cout=1
A = 4'd4; B = 4'd3; Cin = 0; #10; // 7 → SUM=7, Cout=0

$finish;
end
endmodule
```

Output



Question 5

Behavioral Modelling Code

```
module Q5_bcd_to_7seg_behavioral(
    input  [3:0] D,
    output reg [6:0] seg
);
    always @(*) begin
        case (D)
            4'd0: seg = 7'b1111110; // a-f ON, g OFF
            4'd1: seg = 7'b0110000;
            4'd2: seg = 7'b1101101;
            4'd3: seg = 7'b1111001;
            4'd4: seg = 7'b0110011;
            4'd5: seg = 7'b1011011;
            4'd6: seg = 7'b1011111;
            4'd7: seg = 7'b1110000;
            4'd8: seg = 7'b1111111;
            4'd9: seg = 7'b1111011;
            default: seg = 7'b0000000; // blank for invalid codes
        endcase
    end
endmodule
```

Dataflow Modelling Code

```
module Q5_bcd_to_7seg_dataflow(
    input  [3:0] D,
    output [6:0] seg
);

assign seg[0] = (~D[3] & ~D[2] & ~D[1] & D[0]) | // a
               (~D[3] & D[2] & ~D[1] & ~D[0]) |
               ( D[3] & ~D[2] & D[1] & D[0]) |
               ( D[3] & D[2] & ~D[1] & D[0]) |
               ( D[3] & D[2] & ~D[1] & ~D[0]);

assign seg[1] = ( D[2] & D[1] & ~D[0]) | // b
               ( D[3] & D[1] & D[0]) |
               ( D[3] & D[2] & ~D[0]) |
               (~D[3] & D[2] & ~D[1] & D[0]);

assign seg[2] = (~D[3] & ~D[2] & D[1] & ~D[0]) | // c
               ( D[3] & D[2] & ~D[0]) |
               ( D[3] & D[2] & D[1]);

assign seg[3] = (~D[3] & ~D[2] & ~D[1] & D[0]) | // d
               (~D[3] & D[2] & ~D[1] & ~D[0]) |
               ( D[2] & D[1] & D[0]) |
               ( D[3] & ~D[2] & D[1] & ~D[0]);

assign seg[4] = (~D[3] & D[0]) | // e
               (~D[3] & D[2] & ~D[1]) |
               (~D[2] & ~D[1] & D[0]);

assign seg[5] = (~D[3] & ~D[2] & D[0]) | // f
               (~D[3] & ~D[2] & D[1]) |
               (~D[3] & D[1] & D[0]) |
               ( D[3] & D[2] & ~D[1] & D[0]);

assign seg[6] = (~D[3] & ~D[2] & ~D[1]) | // g
               (~D[3] & D[2] & D[1] & D[0]) |
               ( D[3] & D[2] & ~D[1] & ~D[0]);

endmodule
```